

ENGG2020 DIGITAL LOGIC AND SYSTEMS

CHAPTER 4A: COMBINATIONAL LOGIC

By Dr. Anthony Sum
Department of Computer Science and Engineering
The Chinese University of Hong Kong



CONTENTS

- Combinational logic circuit
- Adder and Subtractor
- Comparator
- Decoder and Encoder
- Multiplexer and Demultiplexer
- Tri-state Buffer




DIGITAL CIRCUIT CATEGORIES

- Combinational logic circuits
 - The outputs at any instant of time depend upon the **inputs** present at that time instant
 - **No memory** in these circuits
- Sequential logic circuits
 - The outputs at any instant of time depend upon the **present inputs** as well as the **past inputs/outputs**
 - There are **memory** elements used to store past information
- In this chapter, let's focus on Combinational Logic Circuits

3

COMBINATIONAL CIRCUIT

 - A combinational circuit consists of input variables, logic gates, and output variables
- Combinational logic gates react to the values of the signals at their inputs and produce the value of the output signal



4

EXAMPLE (CODE CONVERSION)

- Design a combinational logic circuit to convert Binary Code Decimal (BCD) to Excess-3 Code

Table 4.2
Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

excess-3 code
start with 0011=3


5

EXAMPLE (CODE CONVERSION)

- Since we have 4 inputs and 4 outputs, **4x 4-variable K-maps** are constructed for w, x, y, and z
- Some of cells are **X** (i.e. "Don't Care") because there are only 10 digits (i.e. 0 ~ 9) in BCD

Table 4.2
Truth Table for Code Conversion Example


Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

 

6

 EXAMPLE (CODE CONVERSION)

- Use the simplified logic functions, the combinational logic circuit can be built as below:



7



BINARY ADDER AND SUBTRACTOR

HALF ADDER (HA)

- A half adder is a 1-bit adder which do not take carry-in into consideration
- The sum of two 1-bit binary numbers A and B, can be represented as $S = A + B$:
- $0 + 0 = 0$
- $0 + 1 = 1$
- $1 + 0 = 1$
- $1 + 1 = 10$, where 1 is known as carry-out bit, C_o

9

HALF ADDER (HA)

- By summarizing the equations, the truth table of HA is shown below:

A	B	C_o	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

For S, it is a XOR operation of A and B


For C_o , it is an AND operation of A and B

- The Boolean functions of HA: $S = \bar{A}B + A\bar{B} = A \oplus B$,
 carry out bit $C_o = AB$


10

HALF ADDER (HA)

- The logic circuit of HA:

 

- The block diagram of HA:

 

put Co to another HA to add it

11

FULL ADDER (FA)

- When the operations require **more than 1 bit**, HA is not useful
 - Carry-out bits from the lower significant bits are not considered/used at the higher bit operations
- By extending the HA, one can implement a **full adder** (FA) which takes a **carry-in** bit as an extra input
 - The carry-out bit of the lower order bit can be connected to the carry-in bit of the immediate higher order bit
- FA becomes the basic unit for a multiple-bit adder

12

FULL ADDER (FA)

- Three inputs:
 - Two 1-bit numbers, A and B
 - One Carry-in, C_{in}
- Two outputs:
 - Sum, S
 - Carry-out, C_o

- The truth table of FA:

- Equations of FA:

$$S = \Sigma(1, 2, 4, 7),$$

$$C_o = \Sigma(3, 5, 6, 7)$$

A	B	C_{in}	C_o	S	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	2
1	1	0	1	0	
1	1	1	1	1	3

13

FULL ADDER (FA)

$$S = \Sigma(1, 2, 4, 7),$$

$$C_o = \Sigma(3, 5, 6, 7)$$

- Simplify the Boolean functions of FA:

	$C_{in}' (0)$	$C_{in} (1)$
$A'B' (00)$		1
$A'B (01)$	1	
$AB (11)$		1
$AB' (10)$	1	

$$S = A'B'C_{in} + A'BC'_{in} +$$

$$ABC_{in} + AB'C'_{in},$$

$$= A \oplus B \oplus C_{in}$$

	$C_{in}' (0)$	$C_{in} (1)$
$A'B' (00)$		
$A'B (01)$		1
$AB (11)$	1	1
$AB' (10)$		1

$$C_o = AB + BC_{in} + AC_{in}$$

14


VERIFICATION OF S IN FA

$S = A \text{ xor } B \text{ xor } C$ (finally need this form)


15

FULL ADDER (FA)

- The logic circuit of FA:

 

- The block diagram of FA:

 

16

SUMMARY OF HA & FA

- HA forms the basic of binary addition
- FA considers the carry-out bit from the lower significant HA as part of the inputs
- HA and FA can be used for multiple-bit addition
- Their block diagrams are frequently used rather than their logic circuit for high level design

17

HALF SUBTRACTOR (HS)

- A half subtractor is a 1-bit subtractor which do not take borrow bit into consideration
- The sum of two 1-bit binary numbers A and B, can be represented as $D_i = A - B$:
- $0 - 0 = 0$
- $0 - 1 = 1$, where we need to indicate a borrowing, as the output borrow bit, B_o
- $1 - 0 = 1$
- $1 - 1 = 0$

18

HALF SUBTRACTOR (HS)

- By summarizing the equations, the truth table of HA is shown below:

A	B	Di	B _o
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

For Di, it is a XOR operation of A and B

For B_o, it is an AND operation of A' and B

- The Boolean functions of HS:


$$Di = A \oplus B,$$

$$B_o = \bar{A}B$$


19

HALF SUBTRACTOR (HS)

- The logic circuit of HS:

 

- The block diagram of HS:

 

20

FULL SUBTRACTOR (FS)

- When the operations require **more than 1 bit**, HS is not useful
 - Borrow-out bits from the lower significant bits are not considered/used at the higher bit operations
- By extending the HS, one can implement a full subtractor (FS) which takes a **borrow-in** bit as an extra input
 - The borrow-out bit of the lower order bit can be connected to the borrow-in bit of the immediate higher order bit
- FS becomes the basic unit for a multiple-bit subtractor

21

FULL SUBTRACTOR (FS)

 $D_i = A - B - B_{in}$
 borrow out bit

- The truth table of FS:

A	B	B_{in}	D_i	B_o
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- The Boolean functions of FS:

$$D_i = \Sigma(1, 2, 4, 7),$$

$$B_o = \Sigma(1, 2, 3, 7)$$

Example: $8-3=5$

```

  1000
- 0011
-----
  0101

```

 $B_{in}: 1110$
 $B_o: 0111$

22

FULL SUBTRACTOR (FS)

$$Di = \Sigma(1, 2, 4, 7),$$

$$Bo = \Sigma(1, 2, 3, 7)$$

- Simplify the Boolean functions of FA:

	$B_{in}' (0)$	$B_{in} (1)$
$A'B' (00)$		1
$A'B (01)$	1	
$AB (11)$		1
$AB' (10)$	1	

$$Di = A'B'B_{in} + A'BB'_{in} +$$

$$ABB_{in} + AB'B'_{in},$$

$$= A \oplus B \oplus B_{in}$$


	$B_{in}' (0)$	$B_{in} (1)$
$A'B' (00)$		1
$A'B (01)$	1	1
$AB (11)$		1
$AB' (10)$		

$$Bo = A'B_{in} + BB_{in} + A'B$$


23

FULL SUBTRACTOR (FS)

- The logic circuit of FS:

 

- The block diagram of FS:

 

24

EXAMPLE (FULL SUBTRACTOR)

- Example: $A - B = 1110101_2 - 0011100_2 = 117_{10} - 28_{10} = 89_{10} = 1011001_2$

A	1	1	1	0	1	0	1
- B	0	0	1	1	1	0	0
Di	1	0	1	1	0	0	1

B_{in}	0	1	1	0	0	0	
B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	
B_o	B_o	B_o	B_o	B_o	B_o	B_o	B_o
B_o	0	0	1	1	0	0	0

25

EXAMPLE (FULL SUBTRACTOR)

- Example: $A - B = 10011000_2 - 01011001_2 = 152_{10} - 89_{10} = 63_{10} = 00111111_2$

A	1	0	0	1	1	0	0	0
- B	0	1	0	1	1	0	0	1
Di	0	0	1	1	1	1	1	1

B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	B_{in}	
B_o	B_o	B_o	B_o	B_o	B_o	B_o	B_o	B_o

26



PARALLEL ADDER AND SUBTRACTOR



PRALLEL ADDERS AND SUBTRACTORS

- Binary additions or subtractions could be implemented in either serial or parallel fashion
- **Serial** addition takes **longer time** to process as at any given time only a pair of bits are processed
- **Parallel** addition is much **faster** as all bits are processed nearly at the same time
- We can use **FA** and **FS** as the basic building blocks




~commercial package

4-BIT FULL ADDER

- Consider a 4-bit FA to process two 4-bit binary numbers,
 - $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$

 - Inputs: 4 bits for A, 4 bits for B, 1 bit for Carry-in (C_{IN})
- Outputs: 4 bits for Sum (S), 1 bit for Carry-out (C_{OUT})




- To build a 4-bit FA, 1x HA and 3x FAs, or 4x FAs are required

29


4-BIT PARALLEL ADDER (HYBRID)

because ha and fa also use

 

30


4-BIT PARALLEL ADDER (STANDARD)

 

31


COMMERCIAL PACKAGE OF 4-BIT ADDER

 - A commercial IC **7483** is a 4-bit parallel adder that implements a FA
- A total of **9 input pins**
 - 4 bits per binary number
 - 1 bit for carry-in
- A total of **5 output pins**
 - 4 bits for the sum
 - 1 bit for carry-out



32


PIN ASSIGNMENT OF 7483

 

33

8-BIT PARALLEL ADDER USING 7483

 - Let's connect the following 2x 7483 to form a 8-bit parallel adder




34

4-BIT FULL SUBTRACTOR

- Consider a 4-bit FS to process two 4-bit binary numbers,
 - $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$
- Inputs: 4 bits for A, 4 bits for B, 1 bit for Borrow-in (B_{in})
- Outputs: 4 bits for Difference (D_i), 1 bit for Borrow-out (B_o)
- To build a 4-bit FA, 1x HS and 3x FSs, or 4x FSs are required


35

4-BIT PARALLEL SUBTRACTOR (HYBRID)

 

36

4-BIT PARALLEL SUBTRACTOR (STANDARD)

 

for dont care, there is no more next digit, so just dont care

PARALLEL SUBTRACTOR USING 2'S COMPLEMENT

- Binary additions can be used for subtractions
- 2's complement** is generated by
 - Flipping the bit values from 1 to 0 or 0 to 1
 - Followed by an addition of 1
- In other words, all high bit subtractor can be implemented using the commercial package parallel adder, such as **7483**

1-BIT SUBTRACTOR USING 2'S COMPLEMENT

- Consider two 1-bit binary numbers, A and B
- Their difference can be expressed as

$$Di = A - B = A + (-B),$$

$$= A + C_2(B) = A + (\bar{B} + 1) = S$$


- where $C_2(B)$ denotes the 2's complement of B
- From the equations, we noticed that
 - Two 1-bit adders are required
 - Three inputs are required, A, B', and 1
 - B' is the 1's complement of B
 - 1 is a HIGH

39

1-BIT SUBTRACTOR USING FA


- The block diagram of 1-bit subtractor, with $C_i = 1$

$$Di = S = A + \bar{B} + 1$$

 


40

4-BIT SUBTRACTOR USING FA

 


41

4-BIT SUBTRACTOR USING FA

 

42

8-BIT SUBTRACTOR USING 7483

 


43

UNIVERSAL 4-BIT ADDER/SUBTRACTOR

- Both adder and subtractor can be implemented by FAs
- Is it possible to have **one single circuit** with a switch to implement both operations?
- Ans: **Yes**, provided that
- If C_{in} at the 1st FA is 1,
 - A subtraction is selected, and
 - The bits of number B will be 1's complemented


44

UNIVERSAL 8-BIT ADDER/SUBTRACTOR

 

control bit to the carry bit
and also help us to determine whether we take carry bit or not

UNIVERSAL 4-BIT ADDER/SUBTRACTOR

 

ANY QUESTIONS ?

47